


Study Problems, Set #8

Spring 2014

[illegible]

1


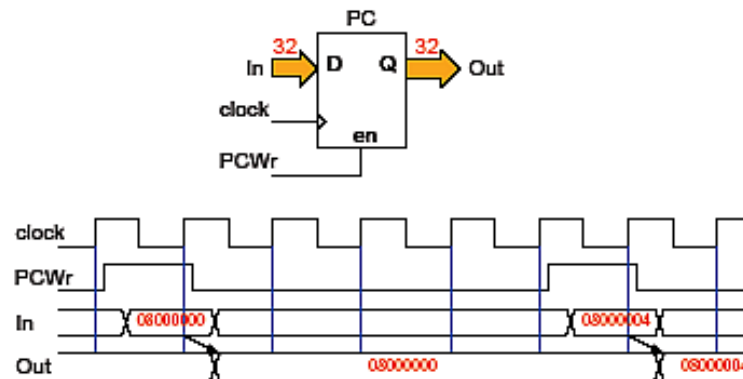
“in” and “out” in the timing diagram correspond to the input to and the output from the PC.]



Assume that:

- $ALUOp = 00$ signals the ALU to *add* A and B.
 $ALUOp = 01$ signals the ALU to *subtract* B from A.
 $ALUOp = 10$ signals the ALU to do the operation specified by the R-format function code.
- $PC+4$ and the *branch target* ($PC+4 + 4 \cdot \text{offset}$) are computed in the IF and ID/RF stages respectively by the ALU. Note that these are computed regardless of the instruction type.

  Complete the following state table for the `lb` and `jr` instructions (state diagram shown below; states 0-5 only). Provide dashes (“-”) for unspecified or don’t care values in the state table. *Note that `jr` is a R-format instruction (see below).*



	0	1	2	3	4	5
IorD						
MemRd						
MemWr						
IRWr						
ALUSrcA						
ALUSrcB						
ALUOp						
PCSrc						
PCWr						
PCWrCond						
RegWr						
RegDst						
MentoReg						
	IF	ID/RF	EX	DM	WB	EX

Solution:

The signals generated during IF and ID/RF are the same for both instructions, `jr` and `lb`. Columns 0-4 in the table shown below give the control signals generated for the `lb` instruction. Column 5 gives the signals generated for the `jr` instruction during the EX stage of that instruction.

	0	1	2	3	4	5
IorD	0	-	-	1	-	-
MemRd	1	-	-	1	-	-
MemWr	0	0	0	0	0	0
IRWr	1	0	0	0	0	0
ALUSrcA	0	0	1	-	-	1
ALUSrcB	01	11	10	-	-	00
ALUOp	00	00	00	-	-	00
PCSrc	00	-	-	-	-	00
PCWr	1	0	0	0	0	1
PCWrCond	-	0	0	0	0	-
RegWr	0	0	0	0	1	0
RegDst	-	-	-	-	0	-
MentoReg	-	-	-	-	1	-
	IF	ID/RF	EX	DM	WB	EX


2. The `jal` (jump and link) instruction requires that `PC+4` is stored in `$RA` before `PC` is set to the jump address. The multi-cycle CPU shown in problem 1 requires a modification to support this instruction.

- (a) In your own words, describe the modifications required in the hardware to implement this instruction. Draw the augmented datapath and highlight all connections required to execute `jal` (assuming the instruction has been loaded into IR).

- (b) Augment the state diagram and the state table in problem 1 for this instruction.


Solution:

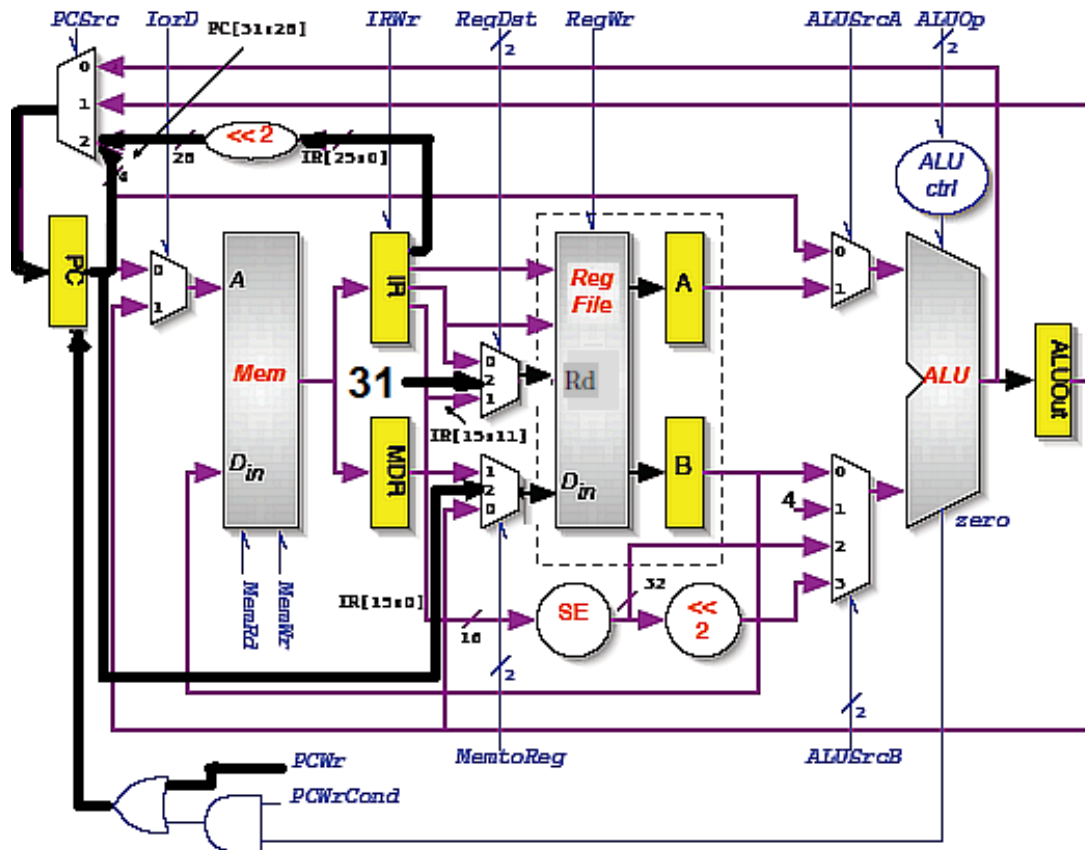- (a) To enable loading $PC+4$ into the register $\$RA$, i.e., the 31st register in the register file, the 2-input multiplexer that determines the destination register must be upgraded to a 3-input multiplexer with the 3rd input hardwired to the value 31. Also, the 2-input multiplexer that determines the data input to the register file (D_{in}) must be upgraded to a 3-input multiplexer, with the 3rd input connected to the register PC. The diagram below shows the augmented datapath. The connections that are required to execute the `jal` instruction are indicated in black bold lines.



- (b) We can now augment the state diagram with a 6th state, as depicted below, to provide the control signals for the execution (EX phase) of the `jal` instruction. The signals generated during IF (phase 0) and ID/RF (phase 1) are the same for all three instructions (`jr`, `lb` and `jal`) and indicated in the state table below. In state 6 (EX phase for `jal`), PC will already contain $PC + 4$, which can be loaded into $\$RA$ by setting the multiplexers such that PC is applied to the register file's D_{in} input and 31 to the register file's Rd input (to write into the 31st register, i.e., register $\$RA$). Simultaneously, $PCSrc = 10$ ensures that PC gets updated with the jump address specified in the `jal` instruction,

stored in register IR.

 

	0	1	2	3	4	5	6
IorD	0	-	-	1	-	-	-
MemRd	1	-	-	1	-	-	-
MemWr	0	0	0	0	0	0	0
IRWr	1	0	0	0	0	0	0
ALUSrcA	0	0	1	-	-	1	-
ALUSrcB	01	11	10	-	-	00	-
ALUOp	00	00	00	-	-	00	-
PCSrc	00	-	-	-	-	00	10
PCWr	1	0	0	0	0	1	1
PCWrCond	-	0	0	0	0	-	-
RegWr	0	0	0	0	1	0	1
RegDst	-	-	-	-	00	-	10
MemtoReg	-	-	-	-	01	-	10
	IF	ID/RF	EX	DM	WB	EX	EX